

Total number of printed pages-7

3 (Sem-3/CBCS) PHY HC 3

2021

(Held in 2022)

PHYSICS

(Honours)

Paper : PHY-HC-3036

(Digital Systems and Applications)

Full Marks : 60

Time : Three hours

**The figures in the margin indicate
full marks for the questions.**

1. Answer the following as directed: $1 \times 7 = 7$

(i) The active components of an IC are

_____ (Fill in the blank)

Contd.

(ii) Which of the following gates cannot be used as an inverter ?

- (a) NOR
- (b) NAND
- (c) X-NOR
- (d) AND

(Choose the correct option)

(iii) The intensity of the spot in a cathode ray tube can be controlled by changing the positive potential on the control grid. *(State True or False)*

(iv) 8421 code is _____ code.
(Fill in the blank)

(v) A flip-flop can store —

- (a) one bit of data
- (b) two bits of data
- (c) three bits of data
- (d) any number of bits of data

(Choose the correct option)

(vi) Each term in the standard SOP form is called a _____. *(Fill in the blank)*

(vii) How many buses are connected as part of the 8085 A microprocessor ?

(a) 3

(b) 4

(c) 5

(d) 6

2. Answer the following questions in brief :

2×4=8

(i) What are linear and digital ICs ? Give examples of them.

(ii) Convert the following decimal numbers into BCD code :

(a) 2579

(b) 29.6

(iii) Write down the Boolean expression for 4 to 1 multiplexer and draw the function table for it.

(iv) What are low and high level languages ? Give examples.

3. Answer **any three** questions from the following : $5 \times 3 = 15$

(i) Convert the following as directed :

(a) Octal 526 to decimal

(b) Octal 356.52 to binary

(c) Hexadecimal 12A to decimal

(ii) Distinguish between combinational circuits and sequential circuits with examples.

(iii) Design a circuit that gives an output $A\bar{B} + \bar{A}B$ using discrete electronic circuits.

(iv) What is race around condition of a JK flip-flop ? How can it be eliminated?

(v) State De Morgan's theorem. Apply De Morgan's theorem to the following expressions :

$$(a) \overline{(A + \bar{B})(\bar{C} + D)}$$

$$(b) \overline{(\bar{A}\bar{B} + \bar{C}\bar{D})(CD + \bar{E}F)}$$

4. Answer **any three** of the following questions:

10×3=30

(i) Draw the block diagram and truth table of a full subtractor. Design a full subtractor logic circuit by using K-map.

5+5=10

(ii) (a) Use the K-map to minimise the following expressions : 6

i. $X = \overline{A}\overline{B} + \overline{B}\overline{C} + \overline{A}C + AB$

ii. $X = \overline{A}\overline{B}\overline{C} + \overline{A}BC + A\overline{B}C + ABC'$

(b) Express the Boolean function $F = BC + \overline{B}A$ in a product of maxterms (POS). 4

(iii) (a) Draw the logic diagram of a master-slave JK flip-flop and explain its operation with the help of a truth table. 6

(b) Distinguish between an encoder and a decoder. 4

(iv) (a) Write down the function of CPU and ALU of a computer.

(b) Distinguish between dynamic RAM and static RAM.

(c) What is a cache memory ? What is its function ?

$$4+3+3=10$$

(v) (a) Draw the block diagram of a microprocessor.

(b) Explain the function of a program counter in a 8085 microprocessor.

(c) Write different flag registers of a 8085 microprocessor.

(d) What are different types of addressing mode in 8085 microprocessor ?

(e) Give an example of a 3-byte instruction.

$$2+3+2+2+1=10$$
